

Al Mansoura University

Faculty of Engineering

Electronics and Communications Dept.

2nd Year Students

Logic Circuit 2

First Semester 2013


Prepared By: Dr. Muhammad Morsy

Chapter 1: Latches

Lecture No. 2

 
1.6- The Edge-Triggered S-R Flip-Flop.

- ✓ The S and R inputs of the S-R flip-flop are called **synchronous inputs** because data on these inputs are **transferred** to the flip-flop's output **only** on the **triggering edge** of the clock pulse.
- ✓ When S is **HIGH** and R is **LOW**, the Q output goes **HIGH** on the triggering edge of the clock pulse, and the flip-flop is **SET**.



 
(a) $S = 1, R = 0$ flip-flop SETS on positive clock edge. (If already SET, it remains SET.)

- ✓ When S is **LOW** and R is **HIGH**, the Q output goes **LOW** on the triggering edge of the clock pulse, and the flip-flop is **RESET**



 (b) $S = 0$. $R = 1$ flip-flop **RESETS** on positive clock edge. (If already RESET, it remains RESET.)

- ✓ When **both** S and R are **LOW**, the output **does not** change from its prior state.



- (c) $S = 0, R = 0$ flip-flop does not change. (If SET, it remains SET; if RESET, it remains RESET.)

✓ An **invalid condition** exists when both S and R are **HIGH**.

Table (1.2) **Truth table** for a positive edge triggered S-R flip-flop.

INPUTS			OUTPUTS		COMMENTS
S	R	CLK	Q	\bar{Q}	
0	0	X	Q_0	\bar{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	?	?	Invalid

↑ = clock transition LOW to HIGH



X = irrelevant ("don't care")

Q_0 = output level prior to clock transition

- ✓ The **operation** and **truth table** for a **negative** edge-triggered S-R flip-flop are the same as those for a **positive edge-triggered** device except that the **falling edge** of the clock pulse is the **triggering edge**.



  Example 1.4: Determine the Q and \bar{Q} output waveforms of the flip-flop shown in the Figure for the S, R, and CLK inputs shown in the Figure. **Assume that the positive edge-triggered flip-flop is initially RESET.**



Solution:


State Table.

CLK No.	S	R	State	Q	\bar{Q}
1	0	0	NC	0	1
2	0	1	Reset	0	1
3	1	0	Set	1	0
4	0	1	Reset	0	1
5	1	0	Set	1	0
6	1	0	Set	1	0

1. At **clock pulse** 1, S is **LOW** and R is **LOW**, so Q does not change, **NC**.
2. At **clock pulse** 2, S is **LOW** and R is **HIGH**, so Q remains **LOW** (**RESET**).
3. At **clock pulse** 3, S is **HIGH** and R is **LOW**, so Q goes **HIGH** (**SET**).
4. At **clock pulse** 4, S is **LOW** and R is **HIGH**, so Q goes **LOW** (**RESET**).
5. At **clock pulse** 5, S is **HIGH** and R is **LOW**, so Q goes **HIGH** (**SET**).

 
6. At **clock pulse 6**, S is **HIGH** and R is **LOW**, so Q stays **HIGH**.

✓ Once Q is determined, \bar{Q} is easily found since it is simply the complement of Q. The resulting waveform, for Q and \bar{Q} are shown in the Figure.



 
1.6.1-A Method of Edge-Triggering.

- ✓ A **simplified** implementation of an **edge-triggered** S-R flip-flop is illustrated in Figure 1-8(a) and is used to demonstrate the concept of **edge-triggering**.
- ✓ The circuit in Figure 1.8 (a) is **partitioned** into **two sections**, one labeled **Steering gates** and the other labeled **Latch**.
- ✓ The **steeling** gates **direct**, or **steer**, the **clock spike** either to the input to gate G_3 or to the input to gate G_4 , **depending on** the state of the S and R inputs.



 (a) A simplified logic diagram for a positive edge-triggered S-R flip-flop

- ✓ One basic type of **pulse transition** detector is shown in Figure 1.8 (b).




(b) A type of pulse transition detector Figure 1.8

- ✓ As you can see, there is a **small delay** on one input to the **NAND gate** so that the **inverted** clock pulse arrives at the gate input a **few nanoseconds** after the true clock pulse.

- ✓ This circuit **produces** a **very short-duration spike** on the positive-going transition of the clock pulse.
- ✓ In a **negative edge-triggered** flip-flop the clock pulse is inverted first, thus producing a narrow spike on the negative-going edge.
- ✓ To **understand** the operation of this flip-flop, begin with the **assumptions** that it is in the **RESET** state ($Q = 0$) and that the S, R, and CLK inputs are all **LOW**. For this condition, the **outputs** of gate G_1 and gate G_2 are both **HIGH**.


- ✓ The **LOW** on the Q output is coupled back into one input of gate G_4 , making the \bar{Q} output **HIGH**.
- ✓ Because Q is **HIGH**, both inputs to gate G_3 are **HIGH** (remember, the output of gate G_1 is **HIGH**), holding the Q output **LOW**.
- ✓ If a pulse is **applied** to the CLK input, the outputs of gates G_1 and G_2 remain **HIGH** because they are disabled by the **LOWs** on the S input and the R input; therefore, there is **no change** in the state of the flip-flop-it remains in the **RESET** state.

 - ✓ Let's now make **S HIGH**, leave **R LOW**, and apply a clock pulse. Figure 1.9 illustrates the **logic level transitions** that take place within the flip-flop for this condition.



- ✓ Because the **S** input to gate G_1 is now **HIGH**, the output of gate G_1 goes **LOW** for a very short time (**spike**) when CLK goes **HIGH**, causing the Q output to go **HIGH**. Both inputs to gate G_4 are now **HIGH** (remember, gate G_2 output is **HIGH** because R is **LOW**), forcing the \overline{Q} output **LOW**.
- ✓ This LOW on \overline{Q} is **coupled** back into one input of gate G_3 , ensuring that the **Q** output will remain **HIGH**. The flip-flop is now in the **SET** state.

 - ✓ Next, let's make S **LOW** and R **HIGH** and apply a clock pulse. Figure 1.10 illustrates the logic level transitions that occur within the flip-flop for this condition.



- ✓ Because the **R input** is now **HIGH**, the positive-going edge of the clock produces a negative-going spike on the output of gate G_2 **causing** the \bar{Q} output to go **HIGH**.
- ✓ Because of this **HIGH** on Q , both inputs to gate G_3 are now **HIGH** (remember, the output of gate G_1 is **HIGH** because of the **LOW** on S), **forcing** the Q output to go **LOW**.
- ✓ This **LOW** on Q is coupled back into one input of gate G_4 , ensuring that Q will remain **HIGH**. The flip-flop is now in the **RESET** state.

- ✓ As with the **gated latch**, an **invalid condition** exists if a clock pulse occurs when both **S** and **R** are **HIGH** at the same time. This is the **major drawback** of the S-R flip-flop.

1.7-The Edge-Triggered D Flip-Flop.

- ✓ The **D** flip-flop is useful when a **single data** bit (1 or 0) is to be stored. The addition of an **inverter** to an **S-R** flip-flop creates a basic D flip-flop, as in Figure 1.11, where a positive edge-triggered type is shown.

 


Figure 1.11

- ✓ Notice that the **flip-flop** in Figure 1.11 has **only one input**, the D input, in addition to the clock.
- ✓ If there is a **HIGH** on the **D input** when a clock pulse is applied, the flip-flop will **SET**, and the **HIGH** on the D input is **stored** by the flip-flop on the **positive-going** edge of the clock pulse.
- ✓ If there is a **LOW** on the **D input** when the clock pulse is applied, the flip-flop will **RESET**, and the **LOW** on the **D input** is stored by the flip-flop on the leading edge of the clock pulse.

- ✓ In the **SET** state the flip-flop is storing a 1, and in the **RESET** state it is storing a 0.
- ✓ The **logical operation** of the positive edge-triggered **D flip-flop** is summarized in Table 1-3.


Truth table for a **positive edge-triggered D flip-flop**.

INPUTS		OUTPUTS		COMMENTS
<i>D</i>	CLK	<i>Q</i>	\bar{Q}	
1	↑	1	0	SET (stores a 1)
0	↑	0	1	RESET (stores a 0)

↑ = clock transition LOW to HIGH

- ✓ The **operation** of a **negative edge**-triggered device is, of course, the same, **except that triggering** occurs on the **falling edge** of the clock pulse.
- ✓ Remember, **Q follows** D at the active or triggering clock edge.

 Example 1.5: Given the waveforms shown in the Figure for the D input and the clock, determine the Q output waveform if the flip-flop starts out **RESET**.



1.8-The Edge-Triggered J-K Flip-Flop.

- ✓ The J-K flip-flop is **versatile** and is a **widely** used type of flip-flop.
- ✓ The functioning of the J-K flip-flop is identical to that of the **S-R flip-flop** in the **SET RESET**, and no-change conditions of operation.
- ✓ The difference is that the **J-K** flip-flop has **no invalid** state as does the **S-R** flip-flop. Figure 1.12 shows the **basic internal** logic for a **positive edge**-triggered J-K flip-flop.

 


Figure 1.12

- ✓ It **differs** from the **S-R** edge triggered flip-flop in that the Q output is **connected back** to the input of gate G_2 and the \bar{Q} output is **connected back** to the input of gate G_1 .

- ✓ The two control inputs are labeled **J** and **K** in honor of **Jack Kilby**, who invented the integrated circuit.
- ✓ A **J-K** flip-flop can also be of the **negative edge**-triggered type, in which case the clock input is inverted.
- ✓ Table 1-4 **summarizes** the **logical operation** of the edge-triggered J-K flip-flop in truth table form.

Table(1-4)



INPUTS			OUTPUTS		COMMENTS
<i>J</i>	<i>K</i>	CLK	<i>Q</i>	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	\bar{Q}_0	Q_0	Toggle

↑ = clock transition LOW to HIGH

Q_0 = output level prior to clock transition

- ✓ Notice that there is **no invalid state** as there is with an S-R flip-flop.
- ✓ The truth table for a **negative edge-triggered** device is identical except that it is **triggered** on the **falling edge** of the clock pulse.

  
Example 1.6: The waveforms shown in the Figure are applied to the J, K, and clock inputs as indicated. Determine the Q output, assuming that the flip-flop is initially **RESET**.



Solution.

State Table

CLK No.	J	K	State	Q	\bar{Q}
0	X	X	Reset	0	1
1	1	1	Toggle	1	0
2	0	0	NC	1	0
3	0	1	Reset	0	1
4	1	0	Set	1	0
5	1	0	Set	1	0

 



1. **First**, since this is a **negative edge**-triggered flip-flop, as indicated by the "**bubble**" at the clock input, the Q **output** will **change** only on the **negative-going** edge of the clock pulse.
2. At the **first clock** pulse, both J and K are **HIGH**; and because this is a **toggle** condition, Q goes **HIGH**.
3. At **clock pulse 2**, a **no-change** condition exists on the inputs, keeping Q at a HIGH level.
4. When **clock pulse 3** occurs, J is **LOW** and K is **HIGH**, resulting in a **RESET** condition; Q goes **LOW**.

5. At **clock pulse 4**, J is **HIGH** and K is **LOW**, resulting in a **SET** condition; Q goes **HIGH**.

6. A **SET** condition still exists on J and K when clock pulse 5 occurs, so Q will remain **HIGH**.

 Example 1.7: The waveforms shown in the Figure are applied to the flip-flop. Determine the Q output, starting in the **RESET** state.




 

State Table

CLK No.	J	K	State	Q	\bar{Q}
0	X	X	Reset	0	1
1	0	0	NC	0	1
2	1	1	Toggle	1	0
3	0	1	Reset	0	1
4	1	0	Set	1	0
5	1	0	Set	1	0
6	1	1	Toggle	0	1
7	0	1	Reset	0	1

 
- ✓ The **Q output** assumes the state determined by the states of the J and K inputs at the positive-going edge (triggering edge) of the clock pulse.
- ✓ A change in J or K after the triggering edge of the clock has no effect on the output, as shown in the Figure.



 1.9-Asynchronous Preset and Clear Inputs

- ✓ For the flip-flops just discussed, the **S-R**, **D**, and **J-K** inputs are **called synchronous inputs** because **data** on these inputs are **transferred** to the flip-flop's output only on the **triggering edge** of the clock pulse: that is **the data** are **transferred synchronously** with the clock.
- ✓ Most **integrated circuit** flip-flops also have **asynchronous inputs**. These are inputs that **affect** the state of the flip-flop **independent** of the clock.

- ✓ They are normally **labeled preset** (PRE) and clear (CLR), or **direct set** (S_D) and **direct reset** (R_D) by some manufacturers.
- ✓ **An active** level on the **PRESET** input will **SET** the flip-flop, and an **active level** on the **CLEAR** input will **RESET** it. A **logic symbol** for a J-K flip-flop with **PRESET** and **CLEAR** inputs is shown in Figure 1.13.



- ✓ These inputs are **active-LOW**, as indicated by the **bubbles**. These **PRESET** and **CLEAR** inputs must both be kept **HIGH** for **synchronous** operation.
- ✓ Figure 1.14 shows the **logic diagram** for an edge-triggered J-K flip-flop with **active-LOW PRESET (PRE)** and **CLEAR (CLR)** inputs.

 


Figure 1.14

- ✓ This figure illustrates basically how these inputs work. As you can see, they may connect so that they override the effect of the synchronous inputs, J , K , and the clock.